

REPORT



인하대학교
INHA UNIVERSITY



과목명 | 논리회로

담당교수 | 최성용

학과 | 컴퓨터공학과


학년 | 2

학번 | 12171661


이름 | 윤혁

제출일 |


3-1) (a)

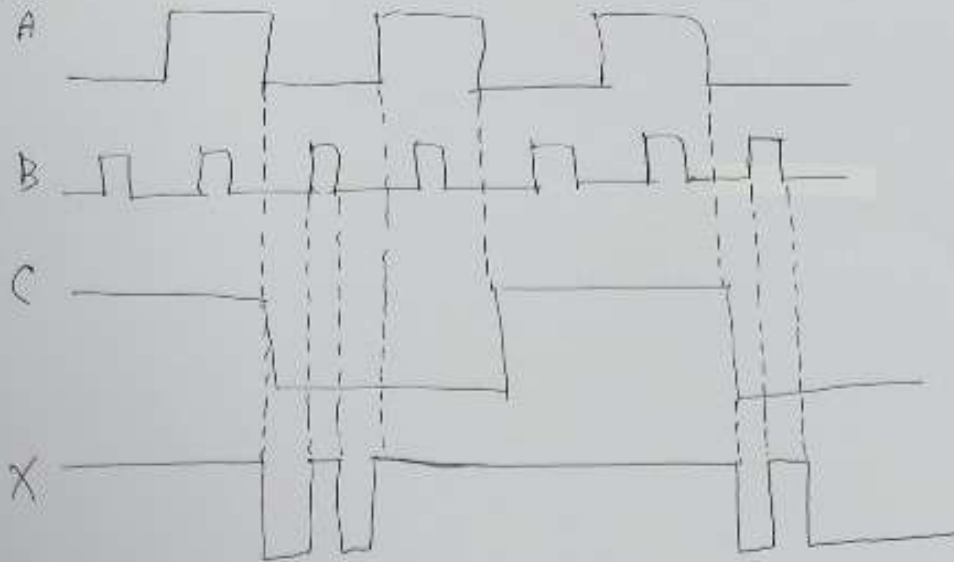

(b)

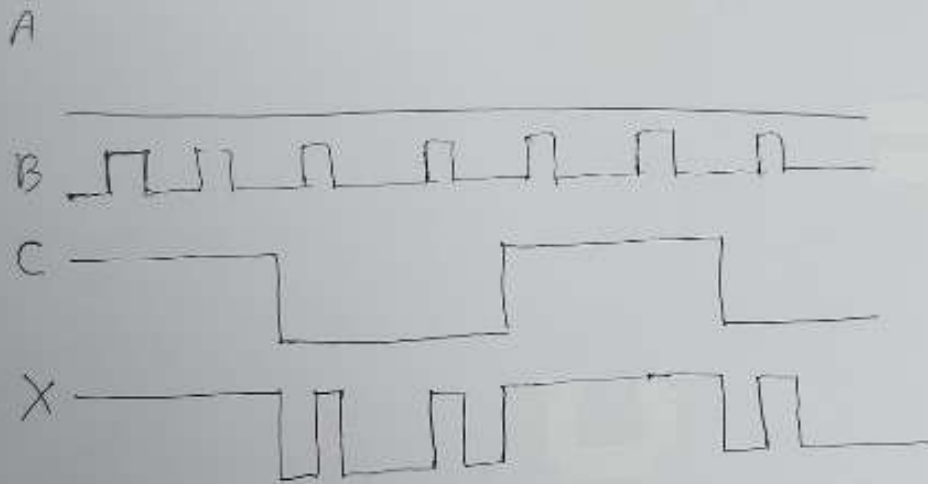

(c)

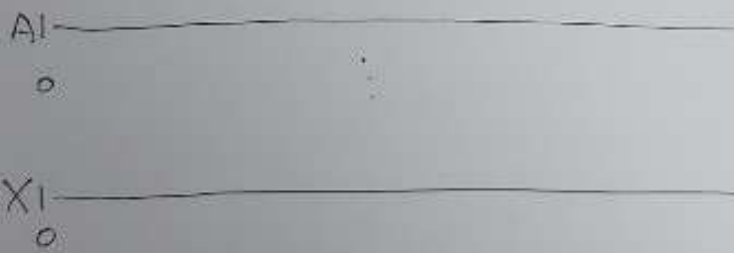

(A가 항상 High이므로 B, C에 관계없이 X는 항상 1이다)

$$\begin{array}{r}
 3-2) \quad 01011100 \\
 + \quad 10001101 \\
 \hline
 11011101
 \end{array}$$

$$\therefore 11011101$$

3-3) (a)

A: 0010010011


B: 1000010000

C: 0000111111

A+B+C


= 1010111111

<timing diagram>

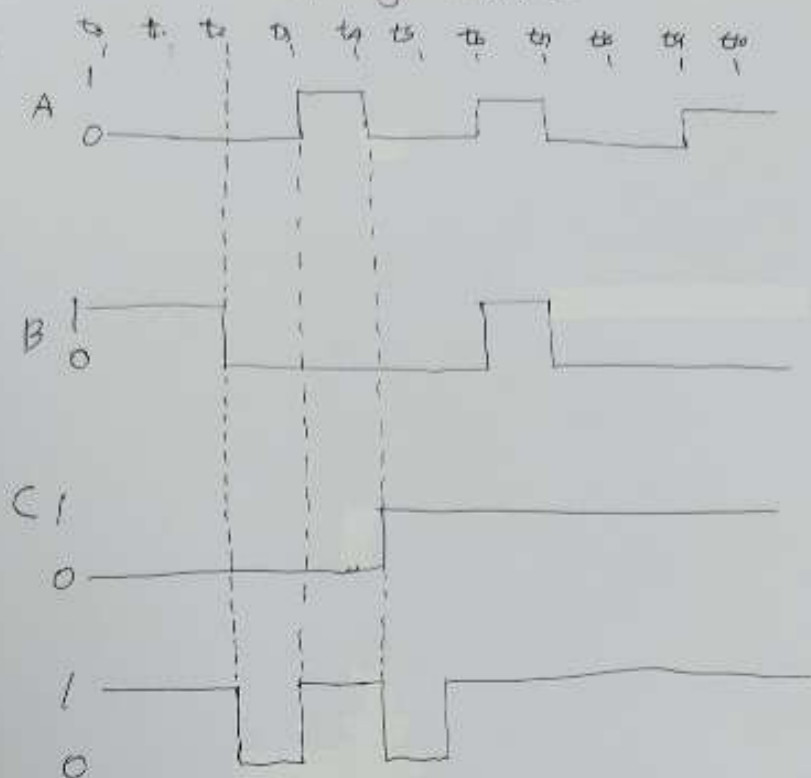

(b)

A: 1001001001

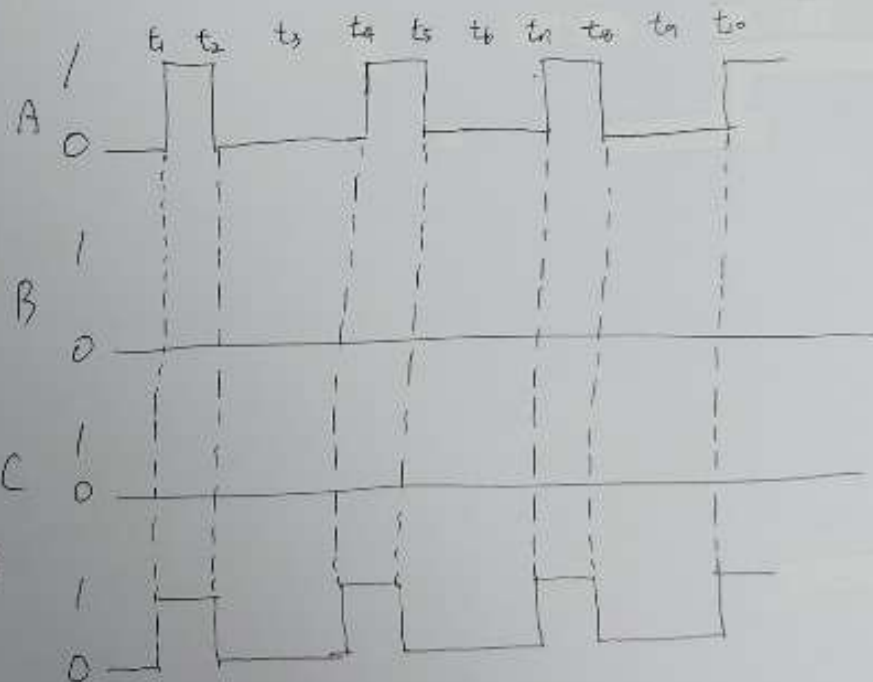

A+B+C = A

= 1001001001


3-5) 1101 1000

X 1100 1101

11001000

= 11001000

3-6)

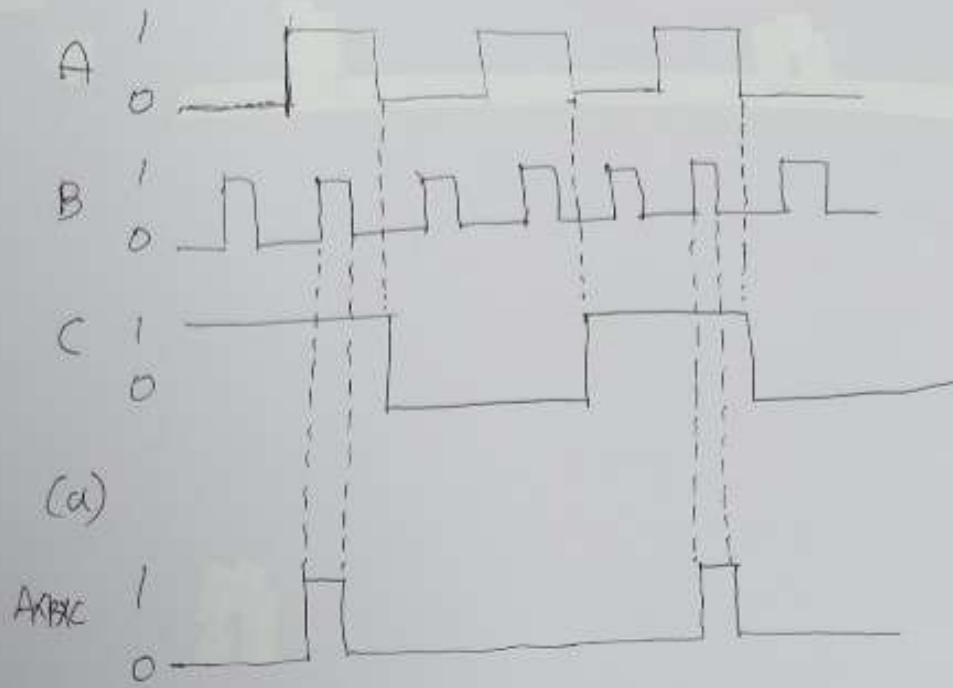

(a)



(b)

A 1

0

이 때

$A \cdot B \cdot C$ 1

0

(c)

A 1

0

이 때

$A \cdot B \cdot C$

1

0

3-9) n-input gate에서 And gate와 OR gate가 같은 결과를 내려면 각각의 two inputs 가 모두 0이거나 1이어야 한다.
 \therefore n개의 inputs이 모두 같아야 한다.

3-12) (a) $(\overline{A+B})BC = X \rightarrow ABC$ (b) $\overline{AB}\overline{C} + \overline{AB}C + \overline{A}BD = X$

<truth table>

| a | b | c | X |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

$$X = \overline{B}(\overline{A}\overline{C} + A\overline{C} + \overline{A}D)$$

$$X = \overline{B}(\overline{C}(\overline{A}+A) + \overline{A}D)$$

$$X = \overline{B}(\overline{C} + \overline{A}D)$$

<truth table>

| a | b | c | d | X |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |

3-14) (a) $X = [D + (\overline{A+B})C] \cdot E$

after AND \leftrightarrow OR, $[D \cdot \overline{AB} + C] + E, D \cdot \overline{AB}C + E$


(b) next page.

3-14) (b)


[illegible]

3-16)


(a) $x = (A+B)CD$

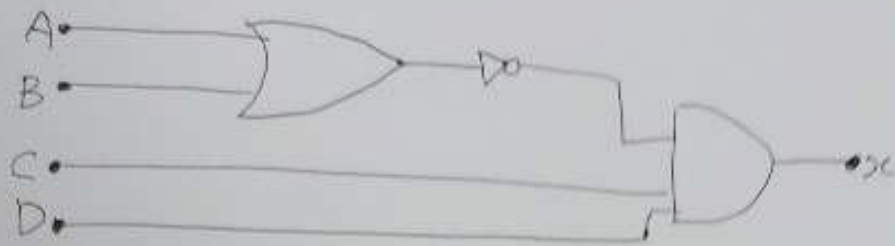


(b) $y = (AB+Z)\overline{D}$

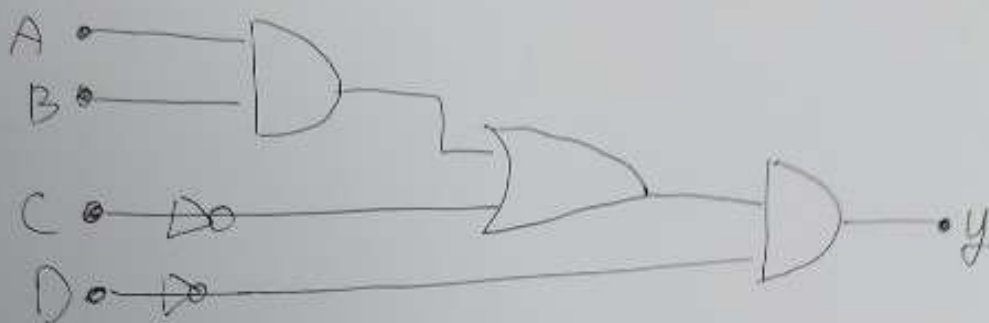

(c) $z = ABZ(A+\overline{B})$

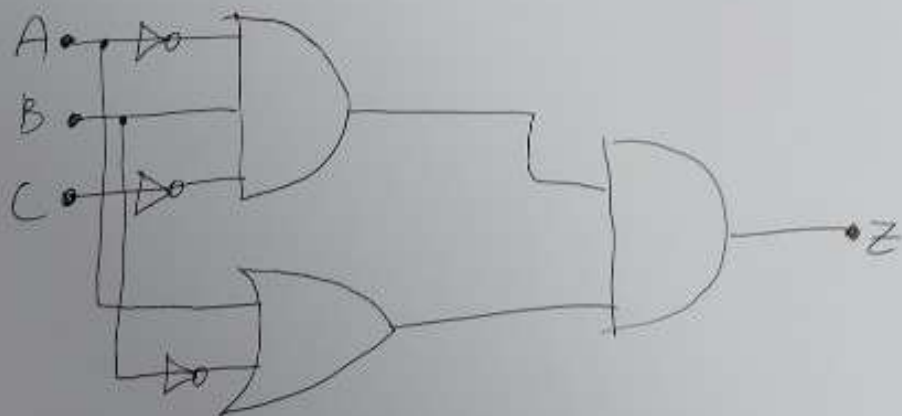

3-18)

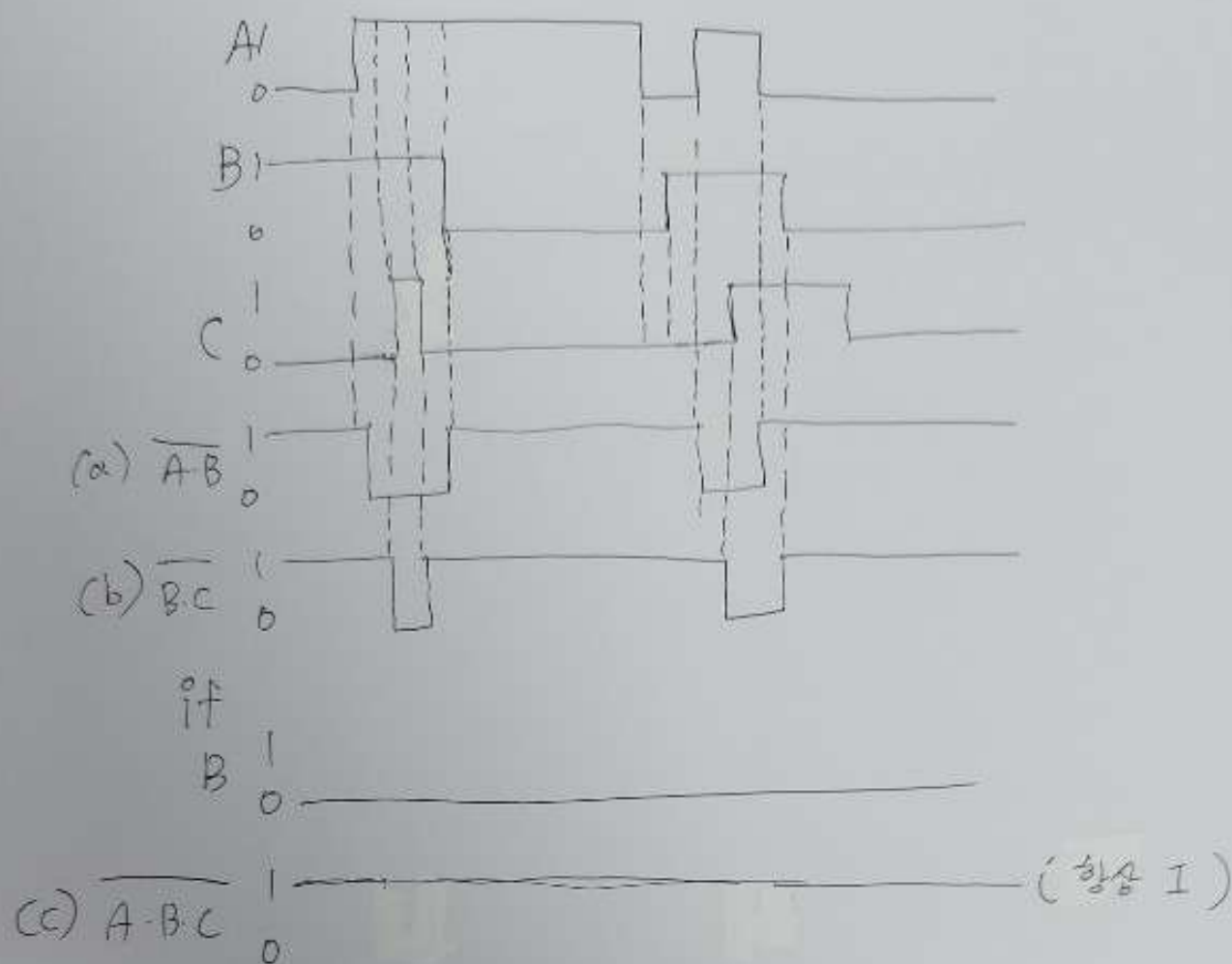

3-23) (a) $A + A = A$, $0 + 0 = 0$, $1 + 1 = 1$

(b) $x \cdot 0 \cdot y = 0$, AND 게이트는 0 이하 하나 이상이면 결과가 0.

(c) $A\overline{B} + A\overline{B} = A$, $A(\overline{B} + B) = A$

(d) $C(C+B) = C$, $0(0+B) = 0$, $1(1+B) = 1$

(e) $x + x\overline{y} = x$, $x(1+y) = x$

(f) $x + 0 + \overline{x} = 1$, $x + \overline{x} = 1$ 이므로 $1 + 0 = 1$

(g) $\overline{A} + A\overline{B} = \overline{A} + \overline{B}$, $(\overline{A} + A)(\overline{A} + B) = \overline{A} + B$

(h) $(x+y)(y+x) = x+y$, $x+y$ 가 2번 곱해지므로 해를 자른다.

(i) $\overline{p} + p\overline{q} = \overline{p} + \overline{q}$, $(\overline{p} + p)(\overline{p} + \overline{q}) = \overline{p} + \overline{q}$

(j) $\overline{xy} + \overline{xy} = 1$, $\overline{(xy)} = \overline{x+y} = \overline{x+y} \rightarrow \overline{x+y} + \overline{x+y} = 1$

$$3-24) (a) x = (m+n)(m+p)(n+p)$$

$$= (\cancel{mm} + mp + n\cancel{m} + np)(n+p)$$

$$= mp\bar{n} + \cancel{mm} + \cancel{np} + \cancel{mp}\bar{p} + n\cancel{m}\bar{p} + \cancel{np}\bar{p}$$

$$= mp\bar{n} + n\bar{m}\bar{p}$$

$$(b) z = \bar{A}B\bar{C} + A\bar{B}\bar{C} + B\bar{C}D$$

$$= \bar{B}\bar{C}(\underbrace{\bar{A} + A}_1 + D)$$

$$= \bar{B}\bar{C}(\underbrace{1 + D}_1)$$

$$= \bar{B}\bar{C}$$

3-26)

$$(a) \overline{\bar{A} + \bar{B} + C} = A\bar{B}\bar{C}$$

$$(b) \overline{\bar{A}\bar{B} + \bar{B}\bar{C}} = \overline{A + \bar{B} + B + \bar{C}} = \overline{A + \bar{C} + 1} = 0$$

$$(c) \overline{(\bar{A} + \bar{B})(A + B)} = (A + B) \cdot \overline{(\bar{A} + \bar{B})} = A + B + AB = A + B$$

$$(d) \overline{\bar{A} + (\bar{B} + \bar{C}) + \bar{D}} = AD(B + C)$$

$$(e) \overline{\bar{A}(\bar{B} + C) \cdot \bar{D}} = A + \bar{B}\bar{C} + D$$



$$(f) \overline{\bar{A} \cdot (\bar{B} + C)} = A + (\bar{B} + C) = A + \bar{B}\bar{C}$$

$$(g) \overline{\bar{A}\bar{B} + A\bar{B}} = \overline{\bar{A}\bar{B}} \cdot \overline{A\bar{B}} = (A + B)(A + B) = A + B$$

$$(h) \overline{\bar{A}\bar{B}(\bar{A} + \bar{B})} = A + B + (A + B) = 1 + 1 = 1$$


$$(i) \overline{(\bar{A} + \bar{B}) + \bar{C}} = (A + B) \cdot C$$

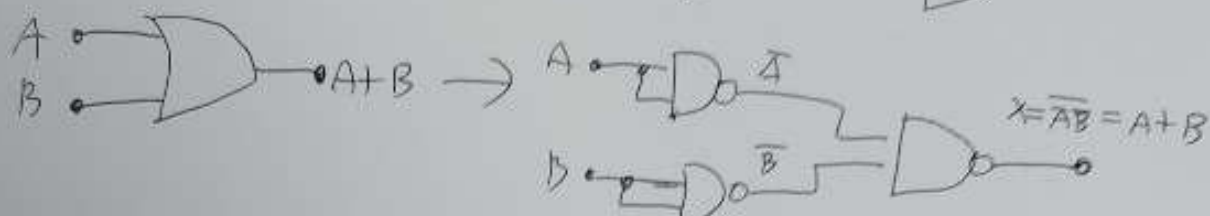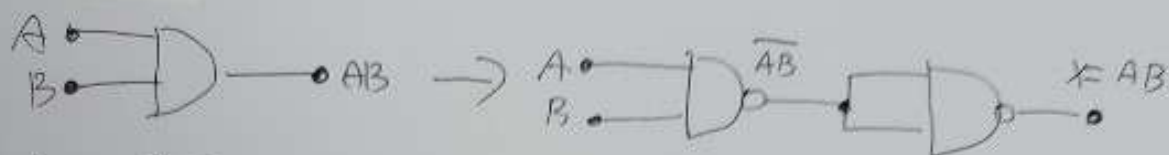3-28) $X = \overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} + \overline{A} \overline{B} D$



ANS $X = (\overline{A} \overline{B} \overline{C}) \cdot (\overline{A} \overline{B} \overline{C}) \cdot (\overline{A} \overline{B} D)$

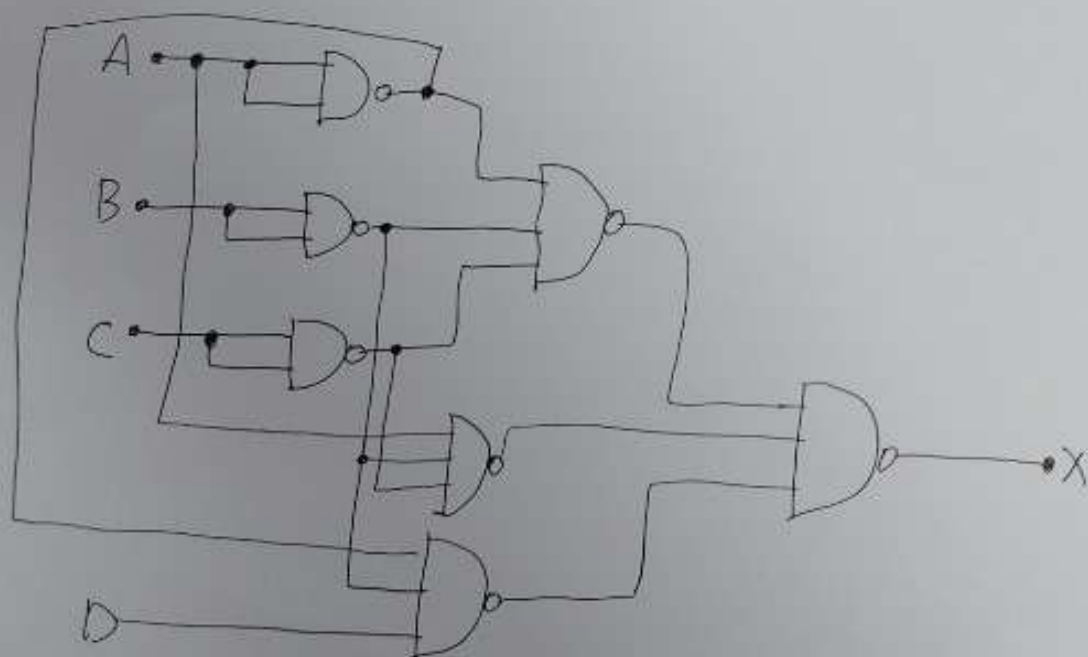
ANS $X = \overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} + \overline{A} \overline{B} D$



3-32) (a) $T=1$ 이고 (P, R) 이 $(0,0)$ 아 $(1,1)$ 아 $(1,0)$ 일때
조종사에게 경고를 준다.

(b) next page

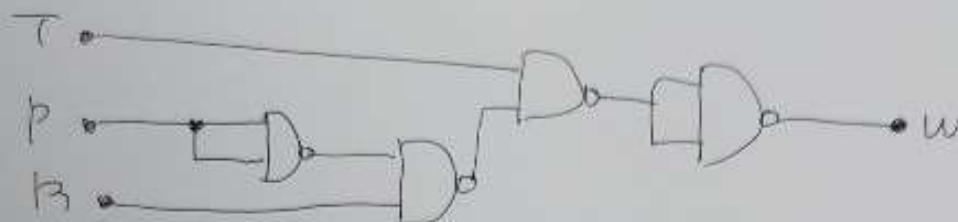
3-32) (b) $W = \overline{\overline{T} (P + B)}$
 $= \overline{\overline{T} (\overline{\overline{P} \overline{B}})}$





- 3-33) (a) If button on ~~trunk lid~~ key fob is pressed AND engine status is motor on)
 OR (engine status is off AND condition of door locks is unlocked
 AND button on trunk lid is pressed)
 OR (engine status is motor on AND condition of door locks
 is unlocked AND button on trunk lid is pressed AND
 parking brake is set), then unlock trunk.


(b) $(F \cdot B \cdot \text{Motor-on}) + (\overline{\text{Motor-on}} \cdot \overline{\text{Locked}} \cdot \text{LID}) + (\text{Motor-on} \cdot \overline{\text{Locked}} \cdot \text{LID} \cdot \text{PBrake})$

(c)

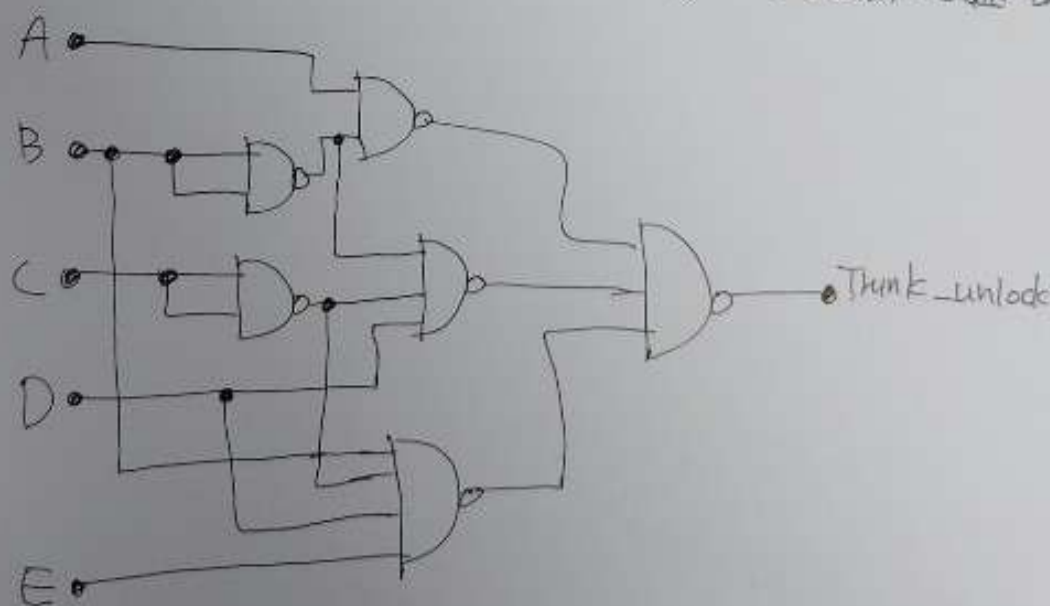

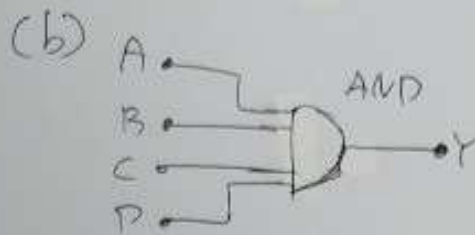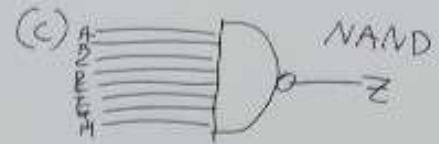

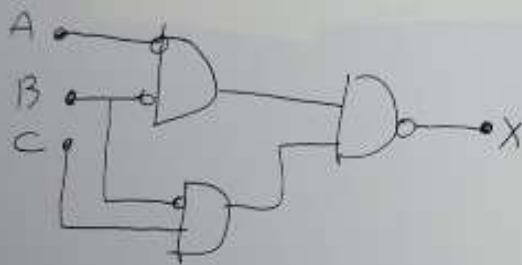3-37) (a) $\overline{(A+B)} \overline{(B+C)}$



(b)


| A | B | C | X |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

$\therefore A(B)가 0 이고 C가 0 일때만$
 1 0 1 0
 1 1 0 1
 1 1 1 0

3-40) A가 1이고 B가 0일때, 또는 B, C 모두 0일때 또는 D가 0 일때
 또는 E가 1 일때 결과가 1일때가 된다.

3-44)

(a)

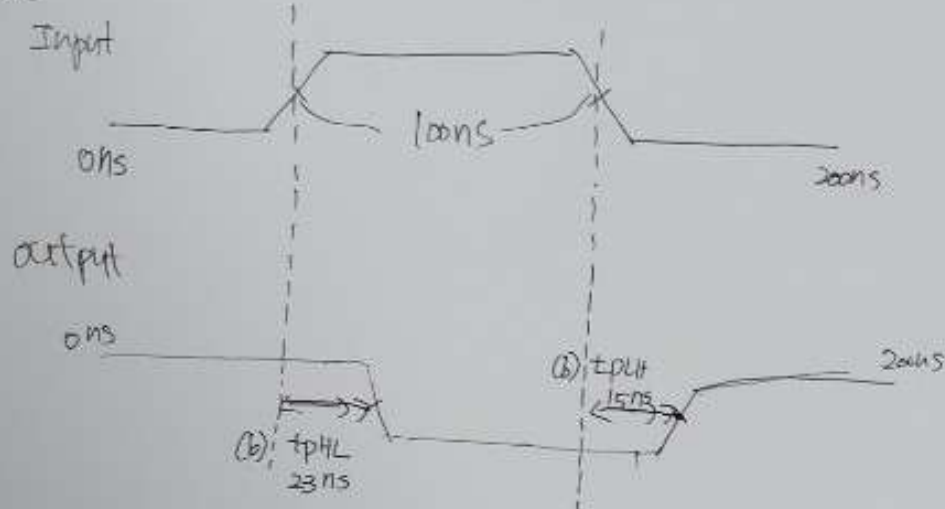

(c) $100\text{ns} - 23\text{ns} + 15\text{ns} = 92\text{ns}$